

Heaven's Light is Our Guide



Rajshahi University of Engineering and Technology
Dept. of Electrical and Computer Engineering

Course Code: ECE-2112

Course Title: Digital Techniques Sessional

Lab Report 02

**Simplification of Boolean Expressions and Verification
Using Logic Circuit Simulation**

Date of Submission: 16 August, 2026

Submitted To:

MST. Mazeda Noor Tasnim
Lecturer,
Dept. of ECE, RUET

Submitted By

Mehedi Rahman Mahi
Roll: 2410015
Reg. No: 1068
Session: 2024-2025

Table of Contents

Table of Contents	2
Task 01: Simplification and Verification of Boolean Expression $F(A, B, C) = A'BC + AB'C + ABC' + ABC$	3
Objective	3
Algebraic Simplification	3
Truth Table	3
Karnaugh Map (K-Map)	3
Circuit Diagram	4
Discussion:	4
Conclusion:	4
Task 02: Simplification and Verification of the Boolean Expression $F(A, B, C) = A(A+B)(A+B+C)$	5
Objective	5
Algebraic Simplification	5
Truth Table	5
Karnaugh Map:	5
Circuit Diagram	6
Discussion	6
Conclusion	6
Task 03: Simplification and Verification of the Boolean Expression $F(A, B, C) = (A + (BC)')(AB + ABC)$	7
Objective	7
Algebraic Simplification	7
Truth Table	7
Karnaugh Map	7
Circuit Diagram	8
Discussion	8
Conclusion:	8
Task 04: Simplification and Verification of the Boolean Expression $F(A, B) = (B'(A + B) + (A + B)(A + B'))B'$	9
Objective	9
Algebraic Simplification	9
Truth Table	9
Karnaugh Map:	9
Circuit Diagram:	10
Discussion	10
Conclusion:	10
References	10

Task 01: Simplification and Verification of Boolean Expression

$$F(A, B, C) = A'BC + AB'C + ABC' + ABC$$

Objective

To reduce a three-variable sum-of-minterms expression to its minimal sum-of-products form, to confirm the reduction using a Karnaugh map, and to verify that the original and simplified circuits are functionally identical by implementing both in Logisim.

Algebraic Simplification

$$\begin{aligned} F(A, B, C) &= A'BC + AB'C + ABC' + ABC \\ &= A'BC + ABC + AB'C + ABC + ABC' + ABC \\ &= BC(A' + A) + AC(B' + B) + AB(C' + C) \\ &= BC + AC + AB \\ &= AB + BC + AC \end{aligned}$$

Truth Table

A	B	C	$F = AB + BC + AC$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Table 01: Truth table for $F(A, B, C) = AB + BC + AC$

Karnaugh Map (K-Map)

A\BC	00	01	11	10
0	0	0	1	0
1	0	1	1	1

Table 02: K-map for $F(A, B, C) = A'BC + AB'C + ABC' + ABC$

Three groups of two adjacent 1-cells are formed: the pair at $BC = 11$ (both rows) gives BC ; the pair at $A = 1, C = 1$ ($BC = 01, 11$) gives AC ; and the pair at $A = 1, B = 1$ ($BC = 11, 10$) gives AB . Combining the three groups yields the minimized expression $F = AB + AC + BC$, matching the algebraic result.

Circuit Diagram

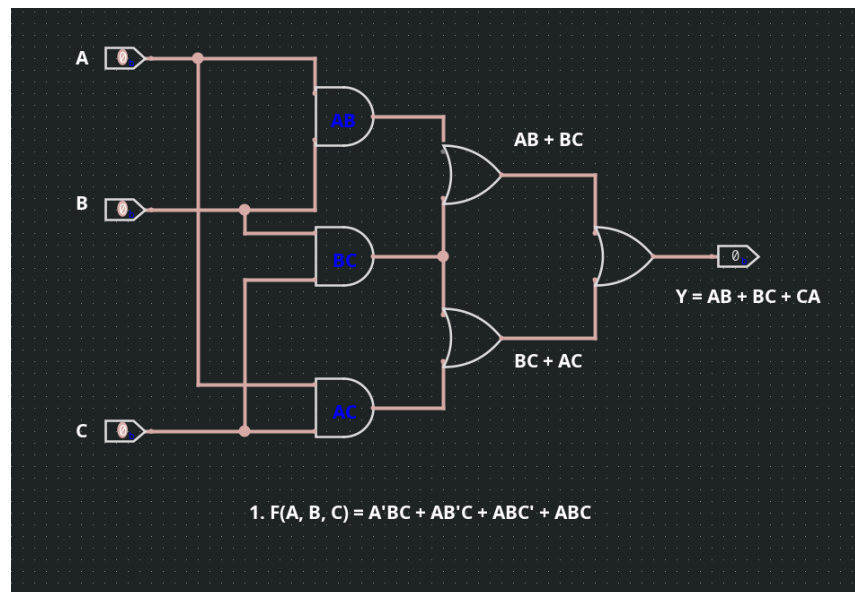


Figure 01: Simplified Circuit Diagram for $F(A, B, C) = A'BC + AB'C + ABC' + ABC$

Discussion

The original circuit uses four 3-input AND gates, inverters, and an OR gate. After simplification, the circuit becomes $AB + AC + BC$, requiring only three 2-input AND gates and an OR gate. Logisim simulation showed that both circuits produced identical outputs, confirming the simplification.

Conclusion

The expression $F = A'BC + AB'C + ABC' + ABC$ was simplified to $F = AB + AC + BC$ using Boolean algebra and a Karnaugh map. Simulation verified that the simplified circuit gives the same output as the original for all input combinations.

Task 02: Simplification and Verification of the Boolean Expression $F(A, B, C) = A(A+B)(A+B+C)$

Objective

To reduce a three-variable product-of-sums-type expression to its simplest form, to confirm the reduction using a Karnaugh map, and to verify the equivalence of the original and simplified circuits in Logisim.

Algebraic Simplification

$$\begin{aligned}
 F(A, B, C) &= A(A + B)(A + B + C) \\
 &= (A + AB)(A + B + C) \\
 &= A(1 + B)(A + B + C) \\
 &= A(A + B + C) \\
 &= A + AB + AC \\
 &= A(1 + B + C) \\
 &= A
 \end{aligned}$$

Truth Table

A	B	C	$F = A$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Table 03: Truth table for $F(A, B, C) = A$

Karnaugh Map

$A \backslash BC$	00	01	11	10
0	0	0	0	0
1	1	1	1	1

Table 04: K-map for $F(A, B, C) = A$

All four cells in the $A = 1$ row are 1, while the entire $A = 0$ row is 0. This forms a single group of four adjacent cells covering the whole row, which eliminates both B and C and leaves only $F = A$, exactly matching the algebraic simplification

Circuit Diagram

Task 03: Simplification and Verification of the Boolean Expression $F(A, B, C) = (A + (BC)')'(AB + ABC)$

Objective

To reduce a mixed AND-OR-complement expression using De Morgan's theorem and Boolean algebra, to confirm the result with a Karnaugh map, and to verify using Logisim that the simplified circuit behaves as a constant.

Algebraic Simplification

$$\begin{aligned}
 F(A, B, C) &= (A + (BC)')'(AB + ABC) \\
 &= (A + B' + C')' AB (1 + C) \\
 &= AB (A'BC) \\
 &= (AA')BC \\
 &= 0
 \end{aligned}$$

Truth Table

A	B	C	F = 0
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Table 05: Truth table for $F(A, B, C) = 0$

Karnaugh Map

A\BC	00	01	11	10
0	0	0	0	0
1	0	0	0	0

Table 06: K-map for $F(A, B, C) = 0$

Every cell of the map is 0, so there are no 1-cells to group. A Karnaugh map with no populated cells represents the constant function $F = 0$, confirming the algebraic result.

Circuit Diagram

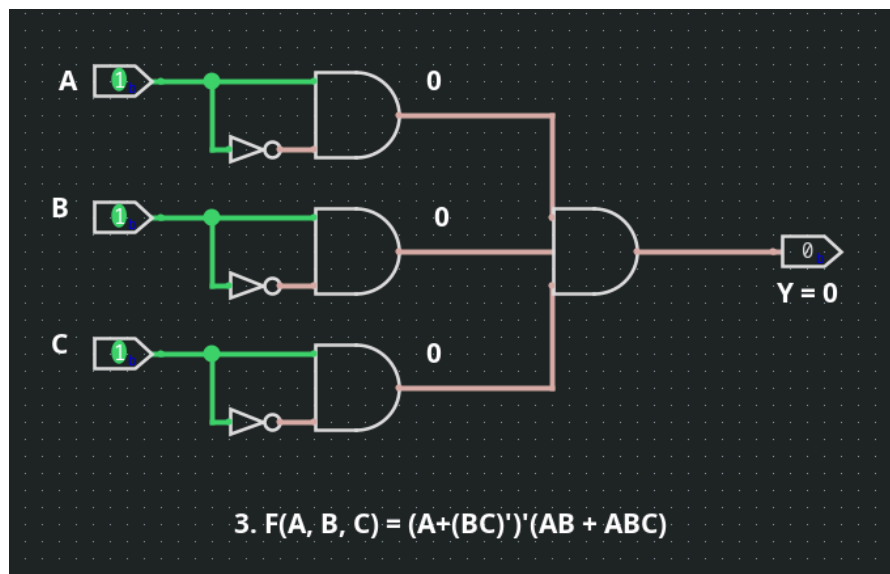


Figure 03: Simplified Circuit Diagram for $F(A, B, C) = (A + (BC)')'(AB + ABC)$

Discussion

Using De Morgan's theorem and the absorption law, the expression simplifies to 0 because it contains the term $A \cdot A' = 0$. Logisim simulation confirmed that the output remains 0 for all input combinations of A, B, and C.

Conclusion

The expression $F = (A + (BC)')'(AB + ABC)$ simplifies to 0. Boolean algebra, Karnaugh map analysis, and Logisim simulation all verified that the output is always logic 0.

Task 04: Simplification and Verification of the Boolean Expression $F(A, B) = (B'(A + B) + (A + B)(A + B'))B'$

Objective

To reduce a two-variable expression built from nested OR and AND terms to its minimal form, to confirm the reduction using a Karnaugh map, and to verify the equivalence of the original and simplified circuits in Logisim.

Algebraic Simplification

$$\begin{aligned}
 F(A, B) &= (B'(A+B) + (A+B)(A+B'))B' \\
 &= B'(AB' + BB' + AA + AB' + AB + BB') \\
 &= B'(AB' + A + AB' + AB) \\
 &= AB'(B' + 1 + B' + B) \\
 &= AB'
 \end{aligned}$$

Truth Table

A	B	$F(A, B) = AB'$
0	0	0
0	1	0
1	0	1
1	1	0

Table 07: Truth table for $F(A, B) = AB'$

Karnaugh Map

A\B	0	1
0	0	0
1	1	0

Table 08: K-map for $F(A, B) = (B'(A + B) + (A + B)(A + B'))B'$

Only a single cell, at $A = 1, B = 0$, is populated. A lone 1-cell cannot be combined with any adjacent cell, so it is read directly as the product of its coordinate literals, giving $F = AB'$, matching the algebraic result.

Circuit Diagram

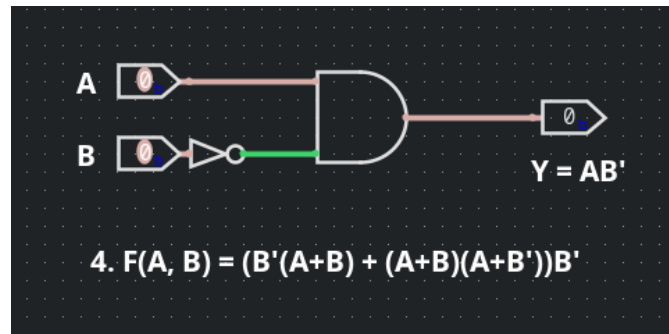


Figure 04: Simplified Circuit Diagram for $F(A, B) = (B'(A+B) + (A+B)(A+B'))B'$

Discussion

Using Boolean algebra, the expression simplifies to $F = AB'$. The simplified circuit requires only an inverter on B and a 2-input AND gate. Logisim simulation confirmed that both the original and simplified circuits produce identical outputs for all input combinations.

Conclusion

The expression $F = (B'(A + B) + (A + B)(A + B'))B'$ was simplified to $F = AB'$. The result was verified using Boolean algebra, a Karnaugh map, and Logisim simulation.

References

- [1] M. M. Mano and M. D. Ciletti, Digital Design, 5th ed. Upper Saddle River, NJ, USA: Pearson, 2013.
- [2] R. J. Tocci, N. S. Widmer, and G. L. Moss, Digital Systems: Principles and Applications, 11th ed. Upper Saddle River, NJ, USA: Pearson, 2011.